

```
1  -----
2  -- Company:          FCEFYN - UNC
3  -- Engineer:         Grupo 03 - ED1
4  --
5  -- Create Date:      20:51:56 05/15/2022
6  -- Design Name:      Trabajo Practico 3
7  -- Module Name:      SumadorRestador4bits - Behavioral
8  -- Project Name:     ALU con FPGA
9  -- Target Devices:   Spartan 3E-100 CP-132
10 -- Tool versions:    Xilinx ISE 14.7
11 -- Description:       Sumador - Restador - AND - OR de 4 bits
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments: (Clock agregado para un control mas estable en las operaciones)
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.STD_LOGIC_ARITH.ALL;
23 use IEEE.STD_LOGIC_UNSIGNED.ALL;
24
25 entity SumadorRestador4bits is
26     Port ( BTN1 : in  STD_LOGIC;
27           BTN2 : in  STD_LOGIC;
28           CLOCK : in  STD_LOGIC;
29           NUM1  : in  STD_LOGIC_VECTOR (3 downto 0);
30           NUM2  : in  STD_LOGIC_VECTOR (3 downto 0);
31           RESULTADO : out STD_LOGIC_VECTOR (3 downto 0);
32           CARRY  : out  STD_LOGIC;
33           NEG    : out  STD_LOGIC );
34 end SumadorRestador4bits;
35
36 architecture Behavioral of SumadorRestador4bits is
37
38     signal aux : STD_LOGIC_VECTOR (3 downto 0) := "0000";
39     signal acarreo : STD_LOGIC := '0';
40     signal negativo : STD_LOGIC := '0';
41
42 begin
43
44     process (CLOCK)
45     begin
46
47         if CLOCK = '1' and CLOCK'event then
48
49             acarreo <= '0';           -- Reseteamos los valores de...
50             negativo <= '0';         -- ...acarreo y negativo para...
51                                     -- ...evitar arrastre del valor.
52
53             if BTN1 = '0' then
54
55                 if BTN2 = '0' then
56
57                     aux <= NUM1 + NUM2;           -- SUMA
```

```
58         if (NUM1 AND NUM2) /= "0000" then      -- Verifica si hubo Acarreo
59             acarreo <= '1';
60         else
61             acarreo <= '0';
62         end if;
63
64     else
65
66         aux <= NUM1 AND NUM2;                    -- AND
67
68     end if;
69
70     else
71
72         if BTN2 = '0' then                        -- OR
73
74             aux <= NUM1 OR NUM2;
75
76         else
77
78             if NUM1 < NUM2 then                    -- Verifica si la resta...
79                 negativo <= '1';                  -- ...dará número negativo...
80                 aux <= NUM2 - NUM1;                -- ...y en ese caso invierte...
81             else                                    -- ...el orden
82                 negativo <= '0';
83                 aux <= NUM1 - NUM2;
84             end if;
85
86         end if;
87     end if;
88 end if;
89 end process;
90
91 RESULTADO <= aux;                                -- Asigna los valores al...
92 CARRY <= acarreo;                                -- ...finalizar el proceso
93 NEG <= negativo;
94
95 end Behavioral;
```